

Project: LED Christmas Tree

Power: USB-C 5V -> MCP73831 charger -> Li-ion 18650 -> Switch -> Astable Multivibrator (3.0-4.2V)
Config: Base resistors R1, R2 = 10k to +BATT; Capacitors C1, C2 = 47µF (Blink rate 2-3 Hz)
USB-C: CC1/CC2 pulled down with 5.1k to GND for standard 5V source detection

